



Practical 8 Measuring the charge stored by a capacitor



Purpose

The aim of this experiment is to measure the charge stored by a capacitor using a coulombmeter and to investigate the formula

$$\text{capacitance} = \frac{\text{charge}}{\text{potential}} \left(C = \frac{Q}{V} \right).$$


Safety

If you are using an electrolytic capacitor, take care to connect it with the correct polarity.

You will need:

- Capacitors ($0.1 \mu\text{F}$, $0.22 \mu\text{F}$, $0.047 \mu\text{F}$)
- Power supply (0–6V dc) (or 6V battery pack and a 10Ω rheostat)
- Digital coulombmeter
- Digital voltmeter
- SPDT switch

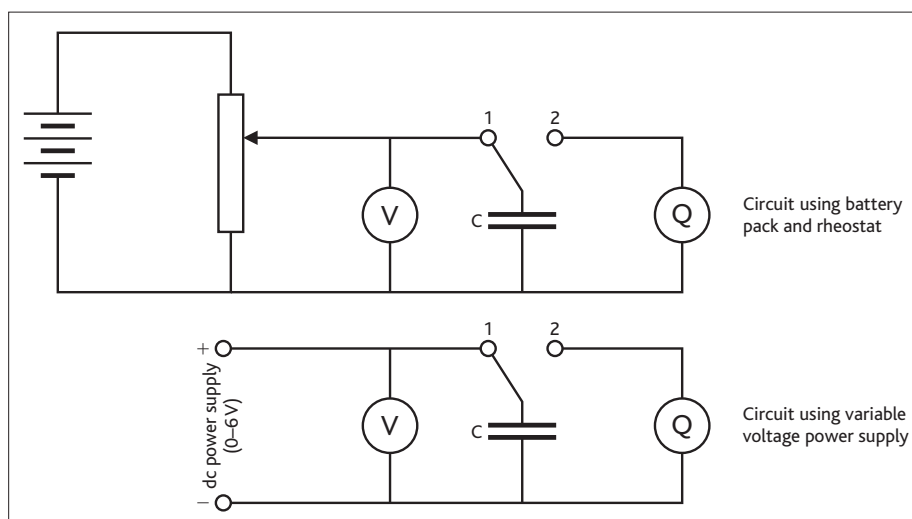


Figure 1: Circuit for measuring the charge stored by a capacitor

Experimental instructions

Connect up the circuit shown in the diagram using the $0.1 \mu\text{F}$ capacitor, with the switch in position 1. Switch on the power supply and adjust the output so that the voltmeter reads 0.5 V.

Move the switch to position 2 and record the reading of charge on the coulombmeter.

Return the switch to position 1, and adjust the voltmeter to read 1.0 V. Move the switch to position 2 and again record the charge.

Repeat the procedure in 0.5 V steps up to a maximum of 6.0 V. Record all your results in a table showing capacitor voltage and charge.

Repeat for different values of capacitance.

Analysis and conclusions

For each capacitor plot a graph of capacitor voltage against charge. Calculate the gradient of each of your graphs and compare this with the stated value of the capacitor.